

# Lecture 18, Nov 17, 2023

## Biasing MOSFET Amplifiers

- To design an amplifier, we have to go through 2 stages:
  - First we set up the circuit to operate at a specific DC configuration
    - \* This determines the *biasing* of the amplifier
    - \* This gives us some parameters that determine the amplifier operation – input/output resistance, voltage gain, and indirectly, the voltage limits
  - We will then use capacitors to inject an AC signal and extract the resulting signal
- Note capital letters are generally pure DC, while lowercase letters are AC
- For a single MOSFET there are generally 3 possible amplifier configurations: common source, common drain, and common gate
  - The “common” terminal is the terminal that is not coupled to an input/output
- There are several ways to do biasing:
  - Fixed  $V_{GS}$  biasing: fixing  $V_{GS}$ , where source and gate are connected to some constant voltage
    - \* This is the simplest, but least useful because it is very sensitive to  $V_{GS}$  and has a small operating range
    - \* The circuit might have a lot of gain, but it will be very sensitive to tolerances
    - \* We are essentially overconstraining the problem
  - Fixed  $V_G$  biasing: fixing  $V_G$  and adding a source resistor
    - \* An increase in current leads to an increased voltage drop across the resistor, which raises  $V_S$
    - \* With a fixed  $V_G$ , this decreases  $V_{GS}$  and decreases the current – this is negative feedback
    - \* This gives us a much wider range of operation –  $V_{IN}$  can be a much larger range and still have good gain
    - \* Introducing the source resistor reduces the output range, which can be fixed using a capacitor, either replacing or in parallel with the source resistor (*bypass capacitor*)
  - Feedback biasing: connect the drain and gate together, with a gate resistor between them
    - \* Since no current flows into the gate at DC, the resistor has no impact on the gate resistance, so we just have  $V_D = V_G$
    - \*  $V_{DG} = 0$  which makes the MOSFET always in saturation (with some limitations)
  - Constant current source (CCS) biasing: connecting a constant current source at the source to set the DC drain/source current
    - \* We can add a bypass capacitor from source to ground, so for AC the capacitor grounds the source
    - \* We can implement the current source using a *current mirror*
- The operating range is restricted due to the modes of the transistors
  - Usually at one end we will get triode mode on some resistors and the other end will give us cutoff mode
  - In both cases we would usually get clipping
- The current mirror shown above behaves equivalently to a constant current source
  - Note the current  $I_{D_1}$  is mirrored in  $I_{D_2}$
  - This only works if the MOSFETs stays in saturation;  $Q_1$  is feedback biased, so it will always be in saturation, but note  $Q_2$  does not have this guarantee
    - \*  $Q_1$  in saturation creates some  $V_{GS}$ , which will be copied exactly by  $Q_2$
    - \* Assuming that  $Q_2$  has the same parameters, we copy the current in  $Q_1$  exactly to  $Q_2$
- Example: design the above circuit so that all transistors operate in saturation, the current source provides 2 mA, and the drain of  $Q_3$  has a quiescent (i.e. bias point) of  $\frac{V_{CC}}{2}$ ; assume  $V_{DD} = V_{SS} = 15\text{ V}$ ,  $k'_n = 4\text{ mA/V}^2$ ,  $W = 250\text{ }\mu\text{m}$ ,  $L = 5\text{ }\mu\text{m}$ ,  $V_T = 4\text{ V}$ 
  - We know that  $Q_3, Q_2$  must have  $I_D = I_S = 2\text{ mA}$ , and due to the current mirror we want  $Q_1$  to have this as well
  - At DC we want the drain voltage to be 7.5 V
  - Starting with the current mirror:

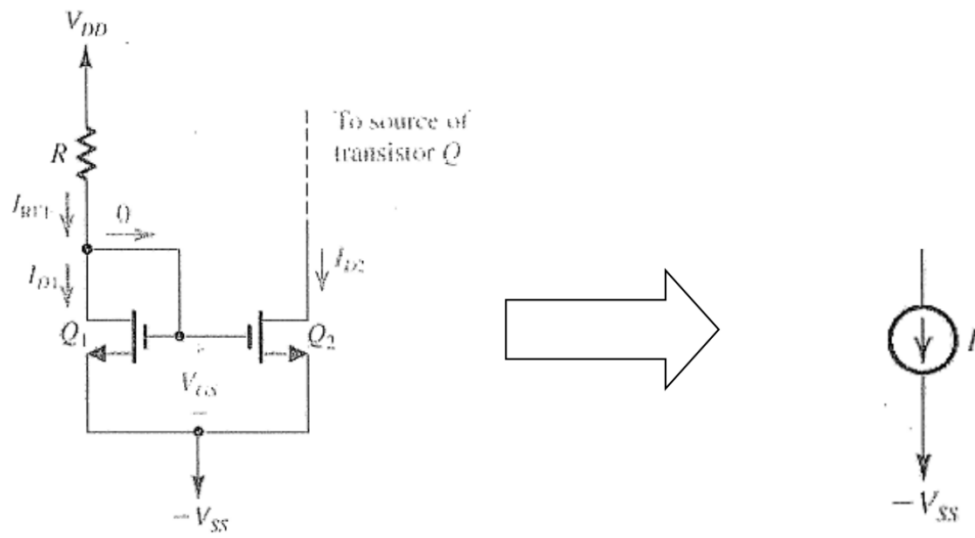


Figure 1: Current mirror circuit.

 


Figure 2: Example circuit using CCS biasing.

- \*  $Q_1$  is always in saturation since  $V_{DG} = 0$
- \*  $I_{D_1} = \frac{1}{2} k'_n \frac{W}{L} (V_{GS_1} - V_T)^2 = 2 \text{ mA}$
- \* We can now solve for  $V_{GS_1} = 4.14 \text{ V}$ , discarding the other result of  $3.86 \text{ V}$  since that gives us cutoff
- \* Note that the current in this branch cannot go through any of the gates, so  $I_{D_1}$  is also the current through  $R_1$
- \* Therefore  $V_{D_1} = V_{G_1} = V_{GS_1} - V_{SS} = -10.86 \text{ V}$  and use this to find  $R_1 = 12.93 \text{ k}\Omega$
- Note  $V_{GS_1} = V_{GS_2}$ , so if  $Q_2$  is in saturation, we will also get  $2 \text{ mA}$  on the right
  - \* We will solve the circuit with this assumption and then check the mode of  $Q_2$  later
- Given that we know  $V_{D_3}$  and  $I_{D_3} = I_{D_2}$  we can solve for  $R_2 = 3.75 \text{ k}\Omega$
- We've already found all component values, but we need to go back and check our assumptions
  - \* For  $Q_3$ ,  $V_{DS_3} = V_{D_3} - V_{S_3}$ ; we need to check if this is greater than  $V_{GS_3} - V_T = V_{GS_2} - V_T$  (since all transistors are the same and must give  $I_D = 2 \text{ mA}$ )
  - \* Since  $V_{GS_3} = V_{GS_2} = 4.14 \text{ V}$ , this gives us  $V_{S_3} = V_{G_3} - V_{GS_3} = 0.86 \text{ V}$  - use this to check that the inequality is satisfied and  $Q_3$  is in saturation
  - \* We also have  $V_{D_2} = V_{S_3} = 0.86 \text{ V}$ , so  $V_{DS_2} = 15.86 \text{ V} > V_{GS_2} - V_T = 0.14 \text{ V}$ , so  $Q_2$  is also in saturation
- Note the saturation mode equation is an approximation since there are other real world effects; in the real world voltages will be slightly different

## Small Signal Amplifiers

- The general idea is that we will couple in an AC signal to our MOSFET circuit using capacitors, which will be amplified
- The DC operating point (biasing) of the amplifier restricts its operating range and also how it behaves as an amplifier - voltage gain, effective resistance, effective source/output resistance
- We will often bias the amplifier to operate "halfway" between the boundaries of cut-off and triode mode

 


Figure 3: Example.

- Example: design the circuit above so that the MOSFET operates halfway between cut-off and triode mode, with  $I_D = 2 \text{ mA}$ ,  $V_T = 0.8 \text{ V}$ ,  $k'_n = 50 \mu\text{A}/\text{V}^2$ ,  $W = 200 \mu\text{m}$ ,  $L = 4 \mu\text{m}$ 
  - The output will idle at some value and any time-changing signal will vary the output level
  - This output level is a function of  $I_D$
  - $R_D$  will give us the drain current and  $R_S$  will shift the DC centre value
  - At the boundary between cutoff and saturation, both equation will apply; we need to get  $V_{DS}$  from these equations

- If  $I_D = 0$ , then  $V_D = V_{DD}$  since no current flows through the resistor, and  $V_S = -V_{SS}$ ; this can give us a value for  $V_{DS}$
- At the boundary of triode,  $V_{DS} = V_{GS} - V_T$
- $V_{DS} = 0.6V_{GS} + 14.6$
- We can get a final condition by using the saturation mode equations
- This gives us  $V_{GS}$  and  $V_{DS}$  and lets us find  $R_S$  and  $V_D$
- Doing this however gets us very skewed limits – we’re very close to cutoff